



Karnaugh Map with Dont Care Conditions



G V V Sharma*

CONTENTS

1 Don't Care Conditions	1
References	3

Abstract—This manual explains Karnaugh maps (K-map) using don't care conditions.

1 DON'T CARE CONDITIONS

1. Don't Care Conditions: 4 binary digits are used in the incrementing decoder [1]. However, only the numbers from 0-9 are used as input/output in the decoder and we *don't care* about the numbers from 10-15. This phenomenon can be addressed by revising the truth table in [1] to obtain Table 1.

2. The revised K-map for A is available in Fig. 2. Show that

$$A = W' \quad (1)$$

3. The revised K-map for B is available in Fig. 3. Show that

$$B = WX'Z' + W'X \quad (2)$$

4. The revised K-map for C is available in Fig. 4. Show that

$$C = X'Y + W'Y + WXY' \quad (3)$$

Z	Y	X	W	D	C	B	A
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	-	-	-	-
1	0	1	1	-	-	-	-
1	1	0	0	-	-	-	-
1	1	0	1	-	-	-	-
1	1	1	0	-	-	-	-
1	1	1	1	-	-	-	-

TABLE 1

5. The revised K-map for D is available in Fig. 5. Show that

$$D = W'Z + WXY \quad (4)$$

6. Verify the incrementing decoder with don't care conditions using the arduino.

7. Display Decoder: Use K-maps to obtain the minimized expressions for a, b, c, d, e, f, g in terms of A, B, C, D with don't care conditions.

Solution:

With Don't Care:

from Fig. 7

$$a = CB'A' + D'C'B'A \quad (5)$$

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

ZY \ XW	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	-	-	-	-
10	1	0	-	-

Fig. 2: K-map for A with don't cares.

ZY \ XW	00	01	11	10
00	0	0	1	0
01	1	1	0	1
11	-	-	-	-
10	0	0	-	-

Fig. 4: K-map for C with don't cares.

ZY \ XW	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	-	-	-	-
10	0	0	-	-

Fig. 3: K-map for B with don't cares.

ZY \ XW	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	-	-	-	-
10	1	0	-	-

Fig. 5: K-map for D with don't cares.

from Fig. 7

$$b = CB'A + CBA' \quad (6)$$

from Fig. 7

$$c = C'BA' \quad (7)$$

from Fig. 7

$$d = CB'A' + CBA + C'B'A \quad (8)$$

from Fig. 7

$$e = A + CB' \quad (9)$$

from Fig. 7

$$f = BA + D'C'A + C'B \quad (10)$$

from Fig. 7

$$g = D'C'B' + CBA \quad (11)$$

8. Verify the display decoder with don't care conditions using arduino.

DC \ BA	BA			
	00	01	11	10
00	0	1	0	0
01	1	0	0	0
11	-	-	-	-
10	0	0	-	-

Fig. 7: K-map for a with don't cares.

DC \ BA	BA			
	00	01	11	10
00	0	0	0	1
01	0	0	0	0
11	-	-	-	-
10	0	0	-	-

Fig. 7: K-map for c with don't cares.

DC \ BA	BA			
	00	01	11	10
00	0	0	0	0
01	0	1	0	1
11	-	-	-	-
10	0	0	-	-

Fig. 7: K-map for b with don't cares.

DC \ BA	BA			
	00	01	11	10
00	0	1	0	0
01	1	0	1	0
11	-	-	-	-
10	0	1	-	-

Fig. 7: K-map for d with don't cares.

REFERENCES

- [1] G V V Sharma, *Karnaugh Map*. [Online]. Available: https://github.com/gadepall/arduino/raw/master/ide/kmap/gvv_kmap.pdf

$DC \backslash BA$	00	01	11	10
00	0	1	1	0
01	1	1	1	0
11	-	-	-	-
10	0	1	-	-

Fig. 7: K-map for e with don't cares.

$DC \backslash BA$	00	01	11	10
00	1	1	0	0
01	0	0	1	0
11	-	-	-	-
10	0	0	-	-

Fig. 7: K-map for g with don't cares.

$DC \backslash BA$	00	01	11	10
00	0	1	1	1
01	0	0	1	0
11	-	-	-	-
10	0	0	-	-

Fig. 7: K-map for f with don't cares.