



# Karnaugh Map



G V V Sharma\*

## CONTENTS

1	Incrementing Decoder	1
2	Karnaugh Map	1

**Abstract**—This manual explains Karnaugh maps (K-map) by finding the logic functions for the incrementing decoder.

### 1 INCREMENTING DECODER

The incrementing decoder takes the numbers 0, 1, ..., 9 in binary as inputs and generates the consecutive number as output. The corresponding truth table is available in Table 0.

Z	Y	X	W	D	C	B	A
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0

TABLE 0

## 2 KARNAUGH MAP

Using Boolean logic, output  $A$  in Table 0 can be expressed in terms of the inputs  $W, X, Y, Z$  as

$$A = W'X'Y'Z' + W'XY'Z' + W'X'YZ' + W'XYZ' + W'X'Y'Z \quad (1)$$

- 1) K-Map for  $A$ : The expression in (1) can be minimized using the K-map in Fig. 1. In Fig. 1, the *implicants* in boxes 0, 2, 4, 6 result in  $W'Z'$ . The implicants in boxes 0, 8 result in  $W'X'Y'$ . Thus, after minimization using Fig. 2, (1) can be expressed as

$$A = W'Z' + W'X'Y' \quad (2)$$

Using the fact that

$$\begin{aligned} X + X' &= 1 \\ XX' &= 0, \end{aligned} \quad (3)$$

derive (2) from (1) algebraically.

**Solution:**

$$A = W'X'Y'Z' + W'XY'Z' + W'X'YZ' + W'XYZ' + W'X'Y'Z \quad (4)$$

$$A = W'X'Y' + W'X'Z' + W'Y'Z' + W'XYZ' \quad (5)$$

$$A = W'X'Y' + W'Z'(X' + Y' + XY) \quad (6)$$

$$A = W'X'Y' + W'Z'((XY)' + XY) \quad (7)$$

$$A = W'Z' + W'X'Y' \quad (8)$$

- 2) K-Map for  $B$ : From Table 0, using boolean logic,

$$B = WX'Y'Z' + W'XY'Z' + WX'YZ' + W'XYZ' \quad (9)$$

Show that (11) can be reduced to

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

ZY \ XW	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	0	0	0	0
10	1	0	0	0

Fig. 1: K-map for A.

ZY \ XW	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	0	0	0
10	0	0	0	0

Fig. 2: K-map for B.

$$B = WX'Z' + W'XZ' \quad (10)$$

using Fig. 2.

- 3) Derive (10) from (11) algebraically using (3).

**Solution:**

$$B = WX'Y'Z' + W'XY'Z' + WX'YZ' + W'XYZ' \quad (11)$$

$$B = WX'Z' + W'XZ' \quad (12)$$

- 4) K-Map for C: From Table 0, using boolean

logic,

$$C = WXY'Z' + W'X'YZ' + WX'YZ' + W'XYZ' \quad (13)$$

Show that (13) can be reduced to

ZY \ XW	00	01	11	10
00	0	0	1	0
01	1	1	0	1
11	0	0	0	0
10	0	0	0	0

Fig. 4: K-map for C.

$$C = WXY'Z' + X'YZ' + W'YZ' \quad (14)$$

using Fig. 4.

- 5) Derive (14) from (13) algebraically using (3).

**Solution:**

$$C = WXY'Z' + W'X'YZ' + WX'YZ' + W'XYZ' \quad (15)$$

$$C = WXY'Z' + X'YZ' + W'YZ' \quad (16)$$

- 6) K-Map for D: From Table 0, using boolean logic,

$$D = WXYZ' + W'X'Y'Z \quad (17)$$

- 7) Minimize (17) using Fig. 6.

- 8) Download the code in

```
wget https://raw.githubusercontent.com/gadepall/arduino/master/7447/codes/inc_dec/inc_dec.ino
```

and modify it using the K-Map equations for A,B,C and D. Execute and verify.

- 9) Display Decoder: Table 9 is the truth table for the display decoder. Use K-maps to obtain the minimized expressions for  $a, b, c, d, e, f, g$  in

ZY \ XW				
	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	0	0	0	0
10	1	0	0	0

Fig. 6: K-map for  $D$ .

terms of  $A, B, C, D$  without don't care conditions.

D	C	B	A	a	b	c	d	e	f	g	Decimal
0	0	0	0	0	0	0	0	0	0	1	0
0	0	0	1	1	0	0	1	1	1	1	1
0	0	1	0	0	0	1	0	0	1	0	2
0	0	1	1	0	0	0	0	1	1	0	3
0	1	0	0	0	1	0	0	1	0	0	4
0	1	0	1	1	0	0	1	1	0	0	5
0	1	1	0	0	1	0	0	1	0	0	6
0	1	1	1	0	0	0	1	1	1	1	7
1	0	0	0	0	0	0	0	0	0	0	8
1	0	0	1	0	0	0	0	1	0	0	9

TABLE 9: Truth table for display decoder.

**Solution:**

Without DON'T CARE:

from Fig. 9

$$a = D'C'B'A + D'CB'A' \quad (18)$$

from Fig. 9

$$b = D'CB'A + D'CBA' \quad (19)$$

from Fig. 9

$$c = D'C'BA' \quad (20)$$

from Fig. 9

$$d = D'CB'A' + D'CBA + C'B'A \quad (21)$$

from Fig. 9

$$e = D'A + C'B'A + D'CB' \quad (22)$$

from Fig. 9

$$f = D'BA + D'C'A + D'C'B \quad (23)$$

from Fig. 9

$$g = D'C'B' + D'CBA \quad (24)$$

DC \ BA				
	00	01	11	10
00	0	1	0	0
01	1	0	0	0
11	0	0	0	0
10	0	0	0	0

Fig. 9: K-map for  $a$ .

DC \ BA				
	00	01	11	10
00	0	0	0	0
01	0	1	0	1
11	0	0	0	0
10	0	0	0	0

Fig. 9: K-map for  $b$ .

$DC$	$BA$			
	00	01	11	10
00	0	0	0	1
01	0	0	0	0
11	0	0	0	0
10	0	0	0	0

Fig. 9: K-map for  $c$ .

$DC$	$BA$			
	00	01	11	10
00	0	1	1	0
01	1	1	1	0
11	0	0	0	0
10	0	1	0	0

Fig. 9: K-map for  $e$ .

$DC$	$BA$			
	00	01	11	10
00	0	1	0	0
01	1	0	1	0
11	0	0	0	0
10	0	1	0	0

Fig. 9: K-map for  $d$ .

$DC$	$BA$			
	00	01	11	10
00	0	1	1	1
01	0	0	1	0
11	0	0	0	0
10	0	0	0	0

Fig. 9: K-map for  $f$ .

		<i>BA</i>			
		00	01	11	10
<i>DC</i>	00	1	1	0	0
	01	0	0	1	0
	11	0	0	0	0
	10	0	0	0	0

Fig. 9: K-map for  $g$ .